

# Introduction to Digital Design and Computer Architecture

## 4. Hardware Description Language

Lilia Kirakosyan

Russian-Armenian University

2025

# Hardware Description Language (HDL)

- **Two leading HDLs:**
  - **SystemVerilog:**
    - Developed in 1984 by Gateway Design Automation.
    - IEEE standard (1364) in 1995.
    - Extended in 2005 (IEEE STD 1800-2009).
  - **VHDL 2008:**
    - Developed in 1981 by the Department of Defense.
    - IEEE standard (1076) in 1987.
    - Updated in 2008 (IEEE STD 1076-2008).

# Simulation and Synthesis

- **Simulation:**

- Inputs applied to circuit.
- Outputs checked for correctness.
- Saves millions of dollars by debugging in simulation instead of hardware.


- **Synthesis:**

- Transforms HDL code into a *netlist*, describing the hardware
  - (i.e., a list of gates and the wires connecting them).

## **IMPORTANT:**

 **When using an HDL, think of the hardware the HDL should produce.**


- **Two types of Modules:**
  - **Behavioral:** Describe what a module does.
  - **Structural:** Describe how it is built from simpler modules.



```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

# SystemVerilog Example with Images

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

 

## Reduction Operators

```
module and8(input  logic [7:0] a,  
            output logic      y);  
    assign y = &a;
```

## Reduction Operators

```
module and8(input  logic [7:0] a,  
            output logic      y);  
    assign y = &a;  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //           a[3] & a[2] & a[1] & a[0];  
endmodule
```



## Conditional Assignment

```
module mux2(input  logic [3:0] d0, d1,  
            input  logic      s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```

# Common SystemVerilog Symbols

Symbol	Meaning
&	Bitwise AND
—	Bitwise OR
	Bitwise NOT
	Bitwise XOR
==	Logical equality
!=	Logical inequality
	Logical AND
——	Logical OR
!	Logical NOT

# Numbers

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsize	decimal	42	00...0101010