

Introduction to Digital Design and Computer Architecture

3. Sequential Logic

Lilia Kirakosyan

Russian-Armenian University

2025

Introduction to Sequential Logic

- Sequential logic circuits have memory.
- Outputs depend on:
 - Current input values
 - Prior states of the system
- Key Definitions:
 - **State**: Information necessary to determine future behavior.
 - **State elements**: Latches and flip-flops storing bits of state.
 - **Synchronous circuits**: Combine logic with a bank of flip-flops.



The state of a circuit influences its future behavior

- State elements store state:
 - Bistable circuit
 - SR Latch
 - D Latch
 - D Flip-flop

Bistable Circuit

Fundamental building block of other state elements

- Two outputs: Q , \bar{Q}
- No inputs

  



Behavior of a Bistable Circuit

Consider the two possible cases:


- **$Q = 0$:** then $Q = 1$, $\bar{Q} = 0$ (consistent)
- **$Q = 1$:** then $Q = 0$, $\bar{Q} = 1$ (consistent)

Stores 1 bit of state in the state variable, Q (or \bar{Q})

  But there are no inputs to control the state.




SR (Set/Reset) Latch

 



SR (Set/Reset) Latch

 - **SR Latch**
- Consider the four possible cases:
 - $S = 1, R = 0$
 - $S = 0, R = 1$
 - $S = 0, R = 0$
 - $S = 1, R = 1$




SR Latch Analysis

  - $S = 1, R = 0$:
then $Q = 1$ and $\bar{Q} = 0$
- $S = 0, R = 1$:
then $Q = 0$ and $\bar{Q} = 1$




SR Latch Analysis

 - $S = 1, R = 0$:
then $Q = 1$ and $\overline{Q} = 0$
- $S = 0, R = 1$:
then $Q = 0$ and $\overline{Q} = 1$




SR Latch Analysis

 - $S = 1, R = 0$:
then $Q = 1$ and $\overline{Q} = 0$
- $S = 0, R = 1$:
then $Q = 0$ and $\overline{Q} = 1$



SR Latch Analysis

 - $S = 1, R = 0$:
then $Q = 1$ and $\overline{Q} = 0$
- $S = 0, R = 1$:
then $Q = 0$ and $\overline{Q} = 1$




SR Latch Analysis

- $S = 1, R = 0$:
then $Q = 1$ and $\overline{Q} = 0$
- Memory!:
- $S = 0, R = 1$:
then $Q = 0$ and $\overline{Q} = 1$
- Invalid State:

SR Latch Symbol

- **SR** stands for *Set/Reset Latch*:
 - Stores one bit of state (Q).
- **Control what value is being stored with S, R inputs:**
 - **Set:** Make the output 1
($S = 1, R = 0, Q = 1$)
 - **Reset:** Make the output 0
($S = 0, R = 1, Q = 0$)

 Must do something to avoid invalid states!



SR Latch Invalid States


- **Invalid State:**

- Occurs when $S = 1, R = 1$.
- This leads to both $Q = 0$ and $\bar{Q} = 0$, violating the fundamental rule that $\bar{Q} \neq Q$.

- **Solution:**

- Avoid $S = 1$ and $R = 1$ inputs in practical implementations.
- Use additional circuitry (e.g., clocked latches or flip-flops) to handle edge cases.

 
Always ensure $S = 0$ or $R = 0$ to maintain valid states.



D Latch Internal Circuit

- The D Latch stores data based on the input D and the clock CLK.
- When CLK = 1:
 - If $D = 0$, $Q = 0$, $\bar{Q} = 1$.
 - If $D = 1$, $Q = 1$, $\bar{Q} = 0$.
- When CLK = 0, the output remains unchanged (previous state is held).


CLK	D	\bar{D}	S	R	Q
0	X				
1	0				
1	1				

 

D Latch Internal Circuit

- The D Latch stores data based on the input D and the clock CLK.
- When CLK = 1:
 - If $D = 0$, $Q = 0$, $\bar{Q} = 1$.
 - If $D = 1$, $Q = 1$, $\bar{Q} = 0$.
- When CLK = 0, the output remains unchanged (previous state is held).


CLK	D	\bar{D}	S	R	Q
0	X	\bar{x}	0	0	Q_{prev}
1	0	1	0	1	0
1	1	0	1	0	1

 

D Flip-Flop



Inputs: CLK , D

 - **Function:**
 - Samples D on the **rising edge** of CLK .
 - When CLK rises from 0 to 1:
 - D passes through to Q .
 - Otherwise, Q holds its **previous value**.
 - Q changes **only** on the rising edge of CLK .
- Called **edge-triggered**.
- Activated on the clock edge.



Flip-Flop Symbols

Registers

  

**THANKS FOR
YOUR ATTENTION**

**AND I HOPE
YOU LIKE IT**

memegenerator.es